



UNIVERSITI
TEKNOLOGI
MALAYSIA
www.utm.my

SCSR1013 DIGITAL LOGIC

MODULE 3: LOGIC GATES

FACULTY OF COMPUTING



Module 3: Overview

NOT Gate (Inverter)
AND Gate
OR Gate
NAND Gate
NOR Gate
Exclusive-OR (XOR) Gate
Exclusive-NOR (XNOR) Gate



- For each gates, we will emphasize on the following:

- i. Characteristics
- ii. Symbols
- iii. Operator
- iv. Boolean expression
- v. Truth Table
- vi. Timing Diagram

Outline

• two logic values either 0 or 1.

- NOT Gate (Inverter)
- AND Gate
- OR Gate




Basic building block

0

1

 - NAND Gate
- NOR Gate
- Exclusive-OR (XOR) Gate
- Exclusive-NOR (XNOR) Gate



Universal gate using
2 of the basic gates



NOT Gate (Inverter)

- Characteristics**



Performs inversion or complementation

- Changes a logic level to the opposite
- 0 (LOW) \rightarrow 1 (HIGH) ; 1 \rightarrow 0

Symbols:

  

  (a) Distinctive shape symbols with negation indicators





(b) Rectangular outline symbols with polarity indicators

Example:

"Output will be 0 if the input is 1"

"Output will be 1 if the input is 0"

  


Continue...


- **Operator**

- NOT Gate is represented by overbar

- **Logic expression**

 

X is the complement of A
X is the inverse of A
X is NOT A

\bar{A} 
"A bar"
"not A"

$X = \bar{A}$ or $X = A'$



OUTPUT is the complement of INPUT
OUTPUT is the inverse of INPUT
OUTPUT is NOT INPUT

Continue...

- Truth table

A	X
0	1
1	0

- Timing diagrams

  


AND Gate


- **Characteristics**

- Performs 'logical multiplication'
 - If all of the input are HIGH, then the output is HIGH.
 - If any of the input are LOW, then the output is LOW.
 - *AND gate must at least have two (2) INPUTs, and must always have 1 (one) OUTPUT. The AND gate can have more than two INPUTs*

- **Symbols**

 

(a) Distinctive shape

 

(b) Rectangular outline with the AND (&) qualifying symbol

- Operator

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$


- Logic operation

$$X = A \cdot B$$

- Truth table

A	B	X = A . B
0	0	0
0	1	0
1	0	0
1	1	1

- Timing Diagram

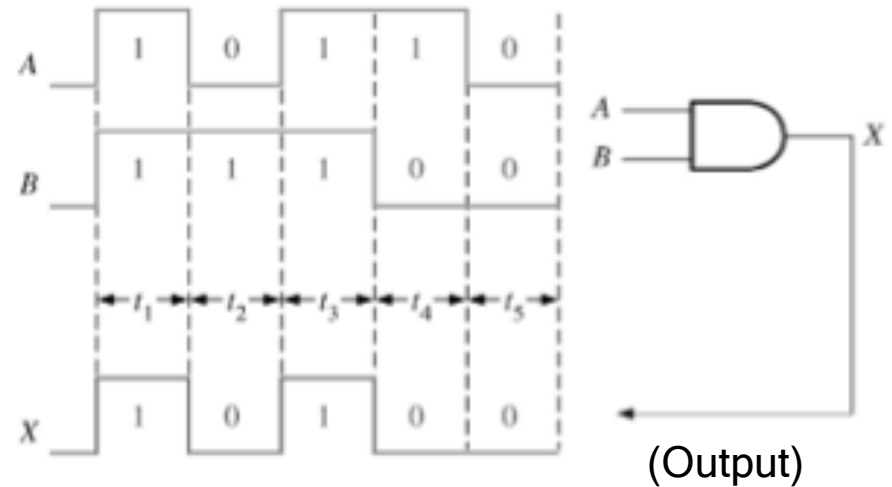


Exercise 3.1:

- Develop the truth table for a 3-input AND gate.
- Determine the total number of possible input combinations for a 4-input AND gate.

Solution:

 (a) Possible input combinations = $2^3 = 8$




(b) Possible input combinations
= $2^4 = 16$


INPUTS			OUTPUT
A	B	C	X
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

(Output 1 when all inputs 1)

 - Performs '*logical addition*'
 - If any of the input are **HIGH**, then the output is **HIGH**.
 - If all of the input are **LOW**, then the output is **LOW**
- Symbols used:



(a) Distinctive shape

 

(b) Rectangular outline with the OR (≥ 1) qualifying symbol



Operator

OR operator can be represented by a plus sign “+”

OR gate performs Boolean addition

Boolean addition follows the basic rules as follows:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1$$

Logical Expression


$$X = A + B$$

Continue...

Truth Table

A	B	$X = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Timing Diagram (DIY)

 


Exercise 3.2:
Draw the output waveform.

Truth Table

A	B	$X = A + B$
0	0	0
0	1	1
1	0	1
1	1	1


Timing Diagram (DIY)

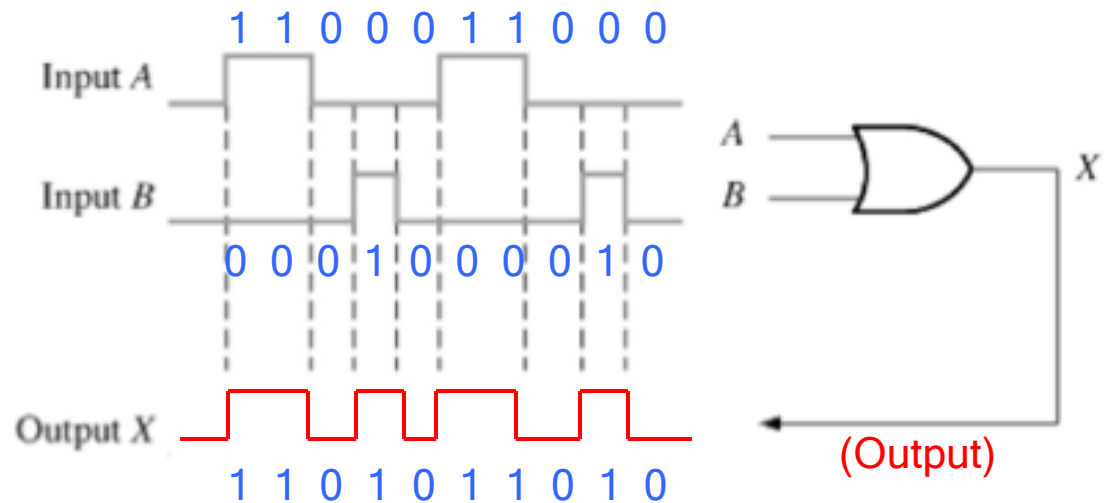


Self-Test:

 - a) Input of a NOT gate is A. If A is LOW, the output is HIGH
- b) If all inputs of an AND gate are LOW, then the output is LOW
- c) If any input of an OR gate is LOW, then the output is HIGH
- d) If A = HIGH, B = LOW, is the logical operation $X = A \bullet B = A + B$ true? NO
- e) From d), what we can do to get X = HIGH ? Invert B
- f) Rewrite the new logical operation from e): $X = A \bullet \bar{B} = A + \bar{B}$

- NAND → NOT-AND ⇒ combines the AND gate and an inverter
- Used as a universal gate
 - Combinations of NAND gates can be used to perform AND, OR and inverter operations
 - If all or any of the input are **LOW**, then the output is **HIGH**.
 - If all of the input are **HIGH**, then the output is **LOW**
- Symbol used:



 (a) Distinctive shape: 2 input NAND gate and its NOT/AND equivalent



(b) Rectangular outline: 2 input NAND gate with polarity indicator

Operator

NAND operator can be represented by a dot with an overbar symbol

$$\overline{0.0} = \overline{0} = 1$$

$$\overline{0.1} = \overline{0} = 1$$

$$\overline{1.0} = \overline{0} = 1$$

$$\overline{1.1} = \overline{1} = 0$$

Logical Expression


$$X = \overline{A \bullet B}$$

Truth Table


INPUTS		OUTPUT	
A	B	AB	$\overline{AB} = X$
0	0	0	$\overline{0.0} = \overline{0} = 1$
0	1	0	$\overline{0.1} = \overline{0} = 1$
1	0	0	$\overline{1.0} = \overline{0} = 1$
1	1	1	$\overline{1.1} = \overline{1} = 0$

Continue...

Timing Diagram (DIY)

 


$$X = \overline{A \cdot B}$$

 


 Exercise 3.3:


Show the output waveform for the 3-input NAND gate below with its proper time relationship to the inputs.



 - NOR → NOT-OR ⇒ combines the OR gate and an inverter
- Used as a universal gate
 - Combinations of NOR gates can be used to perform AND, OR and inverter operations
 - If all or any of the input are **HIGH**, then the output is **LOW**.
 - If all of the input are **LOW**, then the output is **HIGH**
- Symbol used:



 (a) Distinctive shape: 2 input NOR gate and its NOT/OR equivalent



(b) Rectangular outline with the OR (≥ 1) qualifying symbol

Continue...

Operator

NOR operator can be represented by a plus with an overbar symbols

$$\overline{0+0} = \overline{0} = 1$$

$$\overline{0+1} = \overline{1} = 0$$

$$\overline{1+0} = \overline{1} = 0$$

$$\overline{1+1} = \overline{1} = 0$$

Logical Expression



$$X = \overline{A+B}$$

Truth Table

INPUTS		OUTPUT	
A	B	A + B	$\overline{A+B} = X$
0	0	0	$\overline{0+0} = \overline{0} = 1$
0	1	1	$\overline{0+1} = \overline{1} = 0$
1	0	1	$\overline{1+0} = \overline{1} = 0$
1	1	1	$\overline{1+1} = \overline{1} = 0$



Continue...

Timing Diagram (DIY)

  

  Exercise 3.4:

Show the output waveform for the 3-input NOR gate below with its proper time relationship to the inputs.




XOR Gate


- **Characteristics**

- Combines basic logic circuits of AND, OR and Inverter.
- Has only 2 inputs
- Used as a universal gate
 - Can be connected to form an adder that allows a computer to do perform addition, subtraction, multiplication and division in ALU (Arithmetic and Logic Unit).
 - If both of the input are at the same logic level, then the output is LOW.
 - If both of the input are at opposite logic levels, then the output is HIGH

- **Symbol**

 

(a) Distinctive shape

 

(b) Rectangular outline


Continue...

Operator

XOR operator can be represented by a \oplus symbol

Logical Expression
 
$$X = A \oplus B$$
$$= \bar{A}B + A\bar{B}$$



XOR is a combination of 2 AND gates, 1 OR gate, and 2 NOT gates (inverter)


Continue...

Timing Diagram (DIY)

Truth Table

A	B	X = $\overline{A}\overline{B} + \overline{A}B$
0	0	0
0	1	1
1	0	1
1	1	0

X-OR truth table

 


Continue...


Truth Table

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


X-OR truth table

 

 - Has only 2 inputs, but output of XNOR is the **opposite** of XOR
 - If both of the input are at the same logic level, then the output is HIGH.
 - If both of the input are at opposite logic levels, then the output is LOW.
- Symbol used:



(a) Distinctive shape

 

(b) Rectangular outline

Continue...

Operator

XNOR operator can be represented by a \odot symbol


Logical Expression

$$X = A \odot B$$

$$= \overline{A \oplus B}$$

$$= \overline{A\bar{B} + \bar{A}B}$$
 
$$= AB + \overline{A\bar{B} + \bar{A}B}$$





Continue...

XNOR Implementation

- There are two ways in implementing XNOR Gate:
 - The first implementation by **complementing (inverting)** XOR circuit

1

  

$$X = A\bar{B} + \bar{A}B$$




$$X = \overline{A\bar{B} + \bar{A}B}$$

Continue...

Second implementation is by directly implementing the following expression:

2

$$X = AB + \overline{A}\overline{B}$$

 


Continue...

Timing Diagram (DIY)

Truth Table

A	B	X
0	0	1
0	1	0
1	0	0
1	1	1


$$X = AB + \overline{A}\overline{B}$$

 

The characteristic of the above circuit can be proven by the following truth table

Example:

A	B	AB	$\bar{A} \bar{B}$	$X = AB + \bar{A} \bar{B}$
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

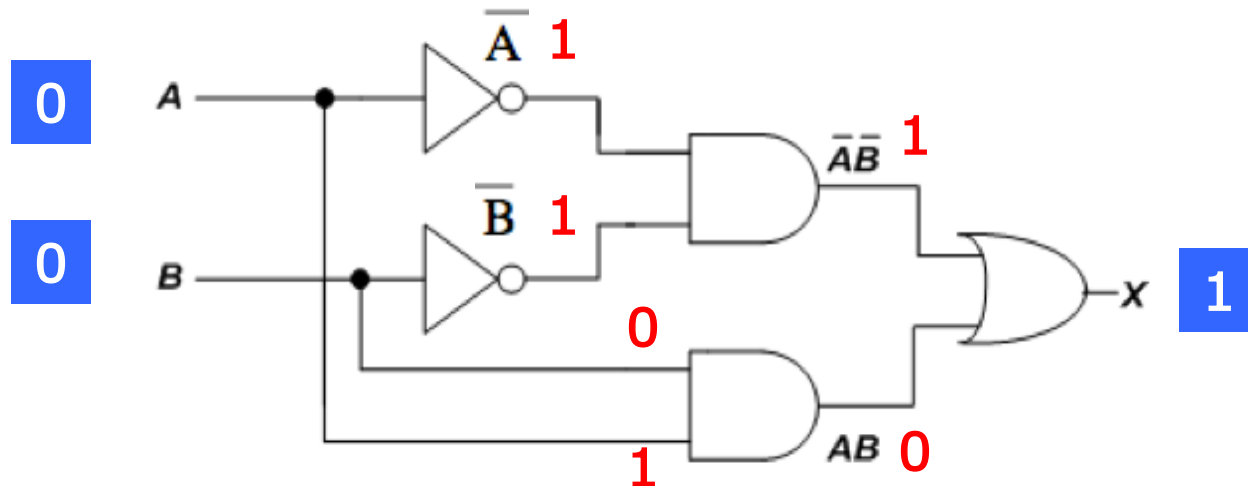

Exercise 3.5:

Determine the output waveforms for the XOR gate and XNOR gate, given the input waveforms, A and B.

